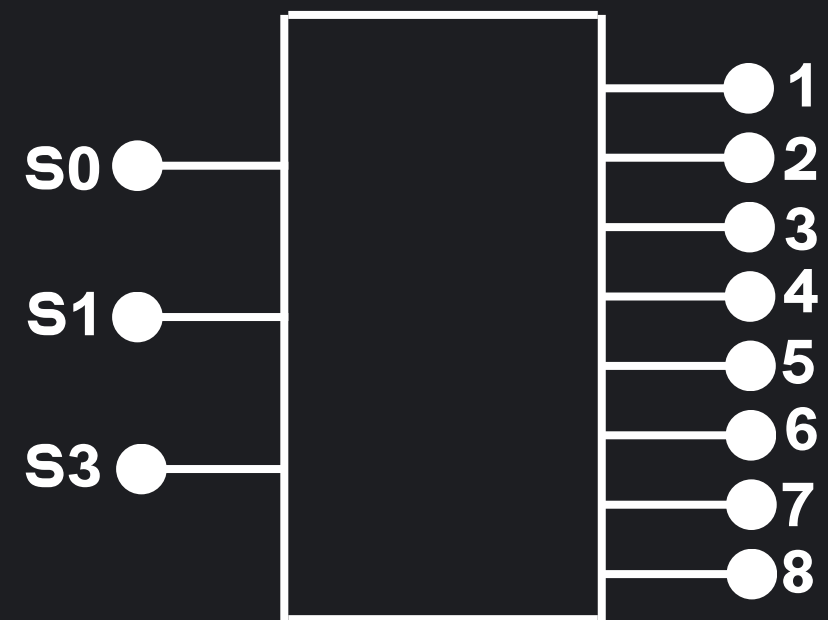


DECODER 3 TO 8




What is a DECODER?


A 3-to-8 Decoder is a basic combinational logic element that converts a 3-bit binary code into one of eight unique output lines. The selected output (representing the decimal value of the inputs) is in a HIGH (1) state, while all other seven non-selected outputs remain in a LOW (0) state.

Q\ how to connect a DECODER ?


Sol:

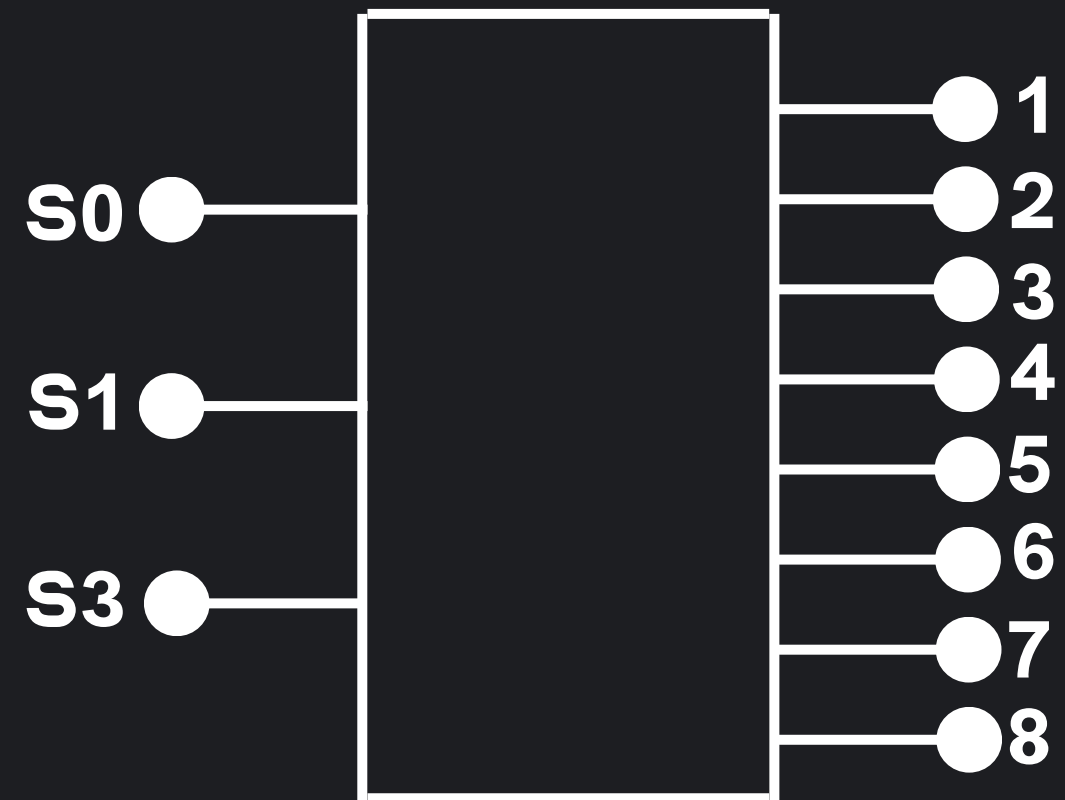


1

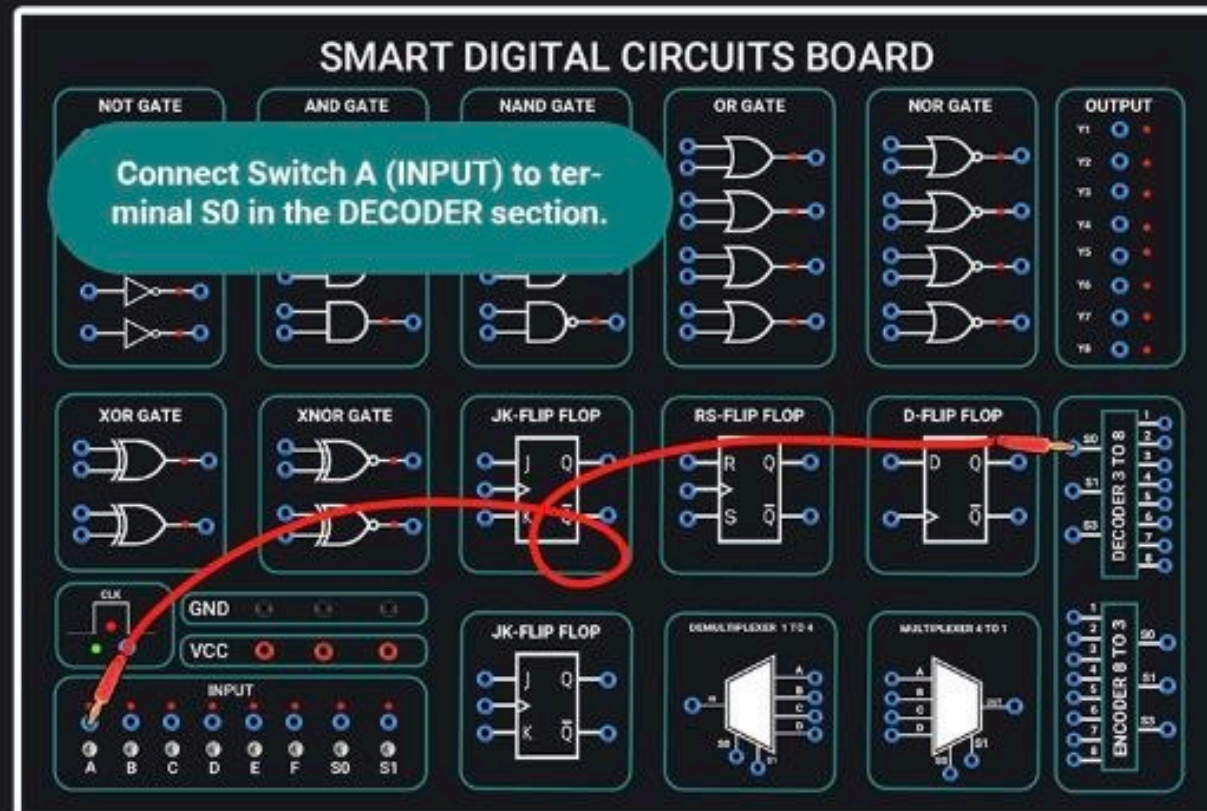


2

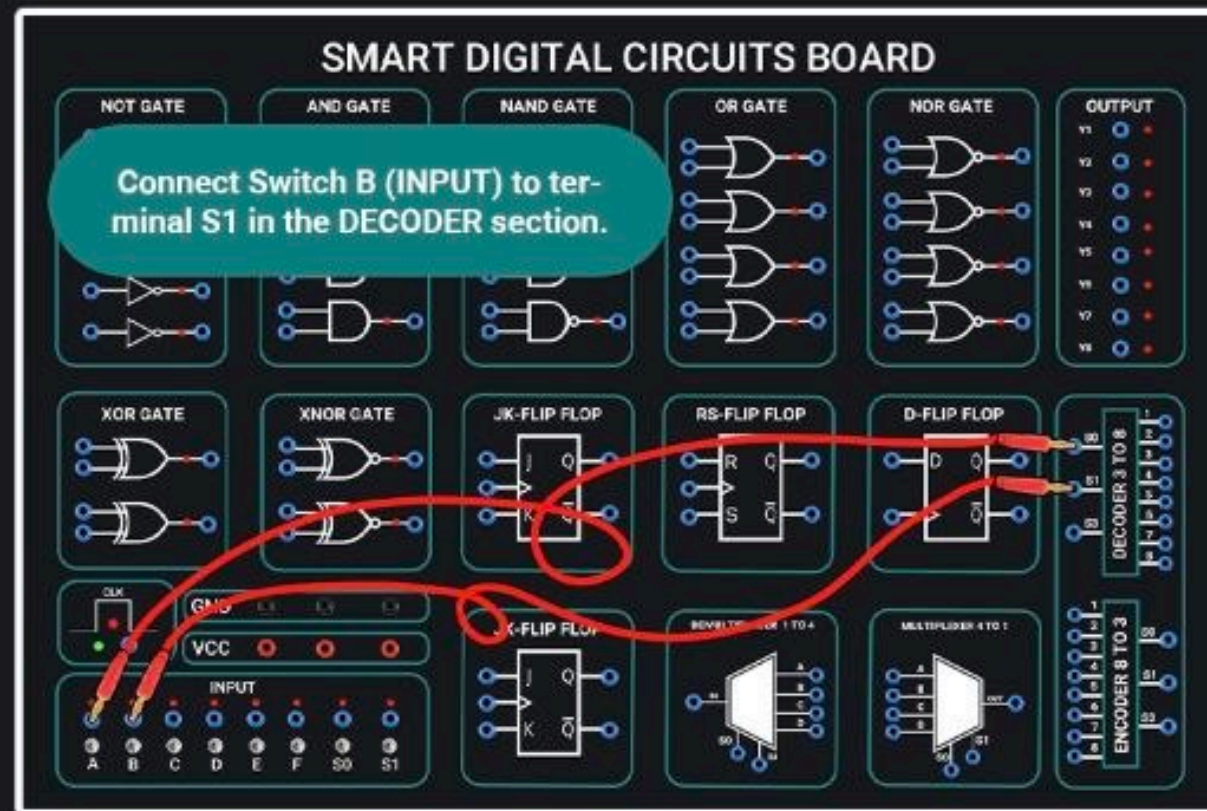

3

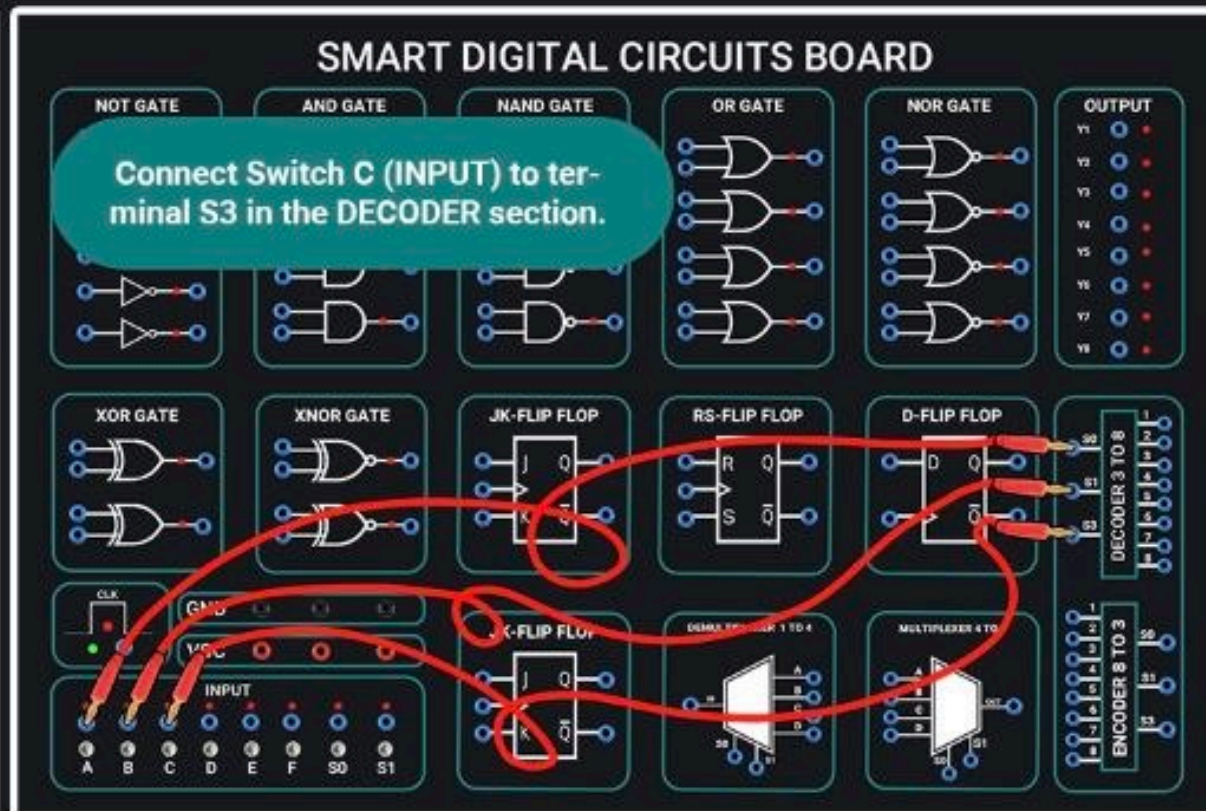

4

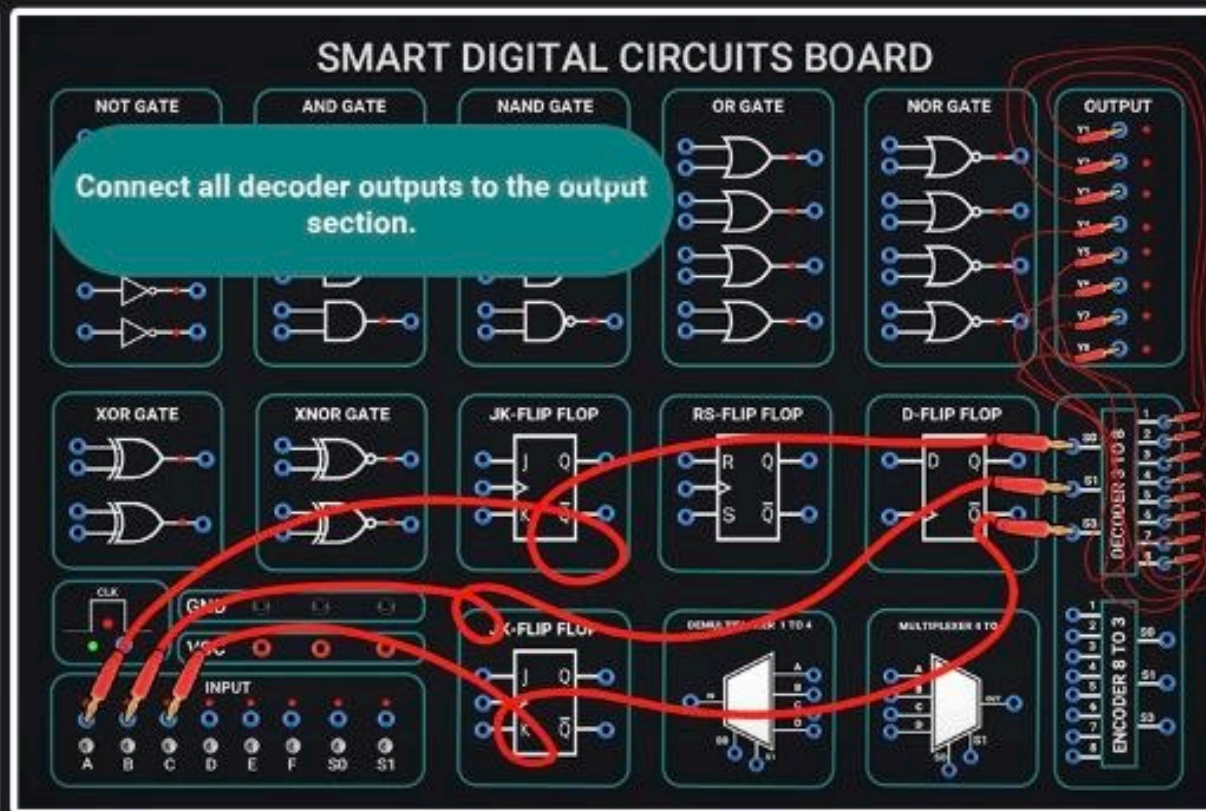

SMART DIGITAL CIRCUITS BOARD

