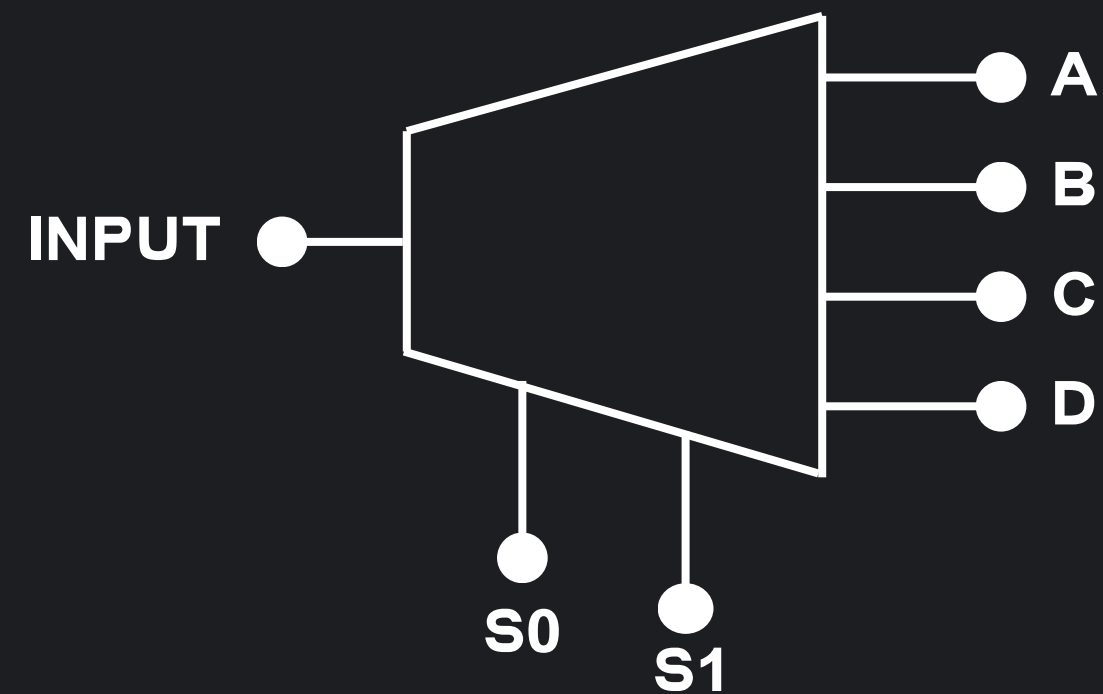



DEMULTIPLEXER 1 TO 4



What is a DEMULTIPLEXER?

A Demultiplexer (DEMUX) is a basic combinational logic element that takes a single input signal and routes it to one of several outputs based on Selector inputs. The selected output is in a HIGH (1) state if the input is HIGH, while all other non-selected outputs remain in a LOW (0) state.

Truth Table

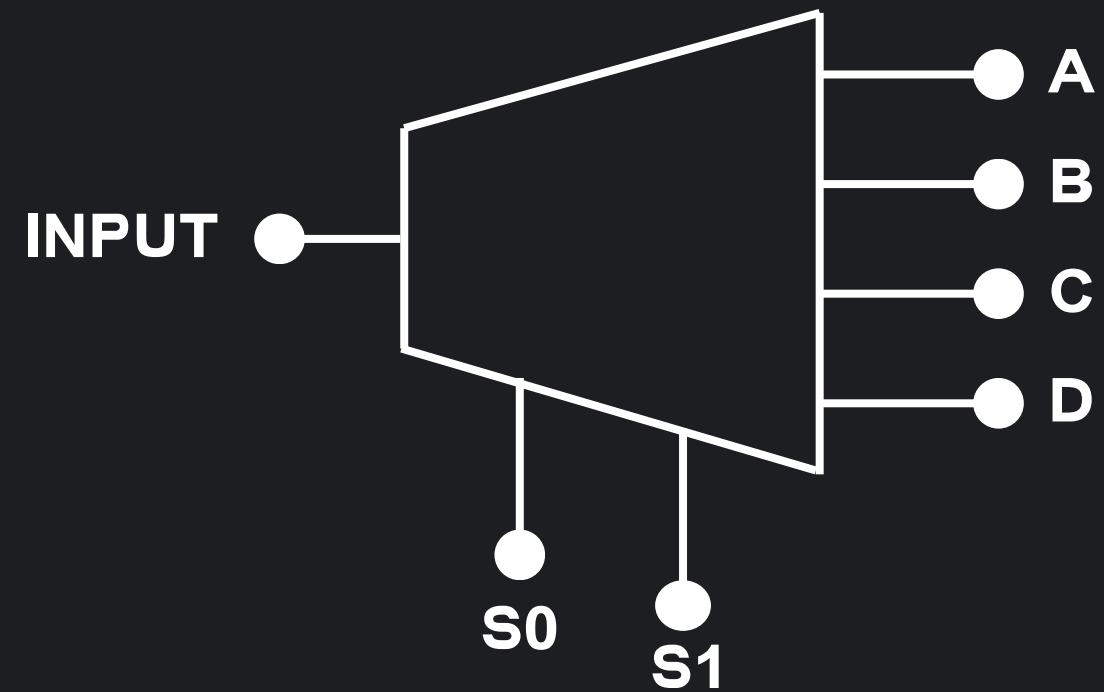

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

Function of the DEMULTIPLEXER

A Demultiplexer performs a logical data distribution operation from a single input to multiple outputs.

The main function of a Demultiplexer is to serve as a digital distribution switch that routes a single input (Data In) to one of several outputs (A, B, C, D) according to this rule:

Output A = Data In when Selectors $S_1_S_0 = 00$.


Output B = Data In when Selectors $S_1_S_0 = 01$.

Output C = Data In when Selectors $S_1_S_0 = 10$.

Output D = Data In when Selectors $S_1_S_0 = 11$.


Q\ how to connect a DEMULTIPLEXER, write the Truth Table.

Sol:

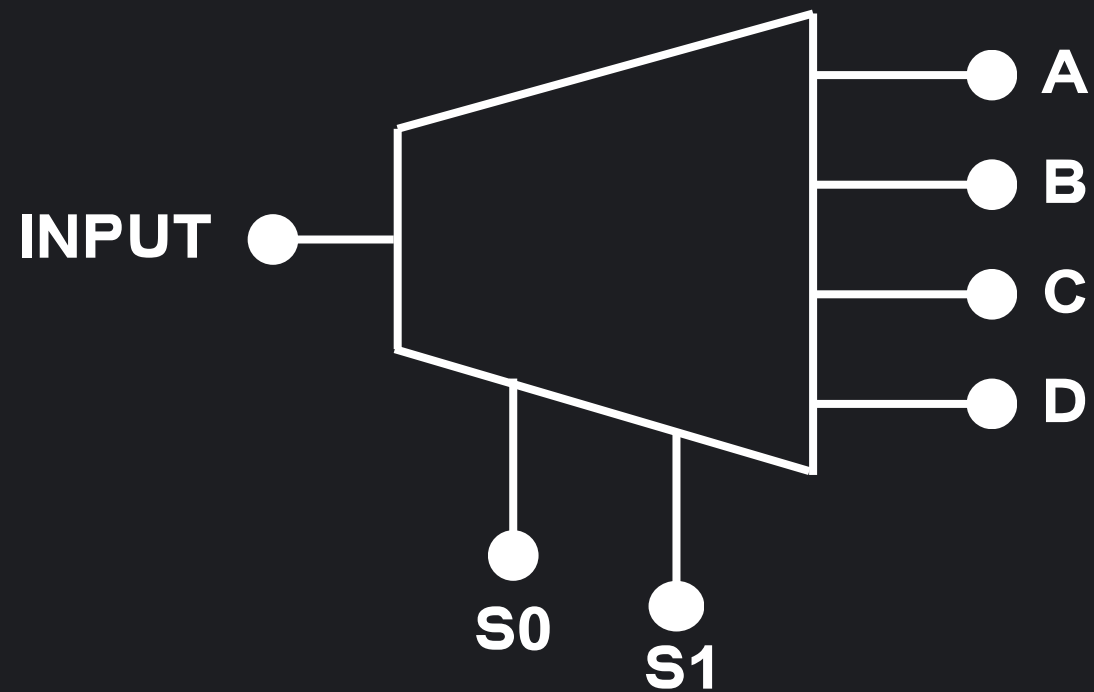


S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

1

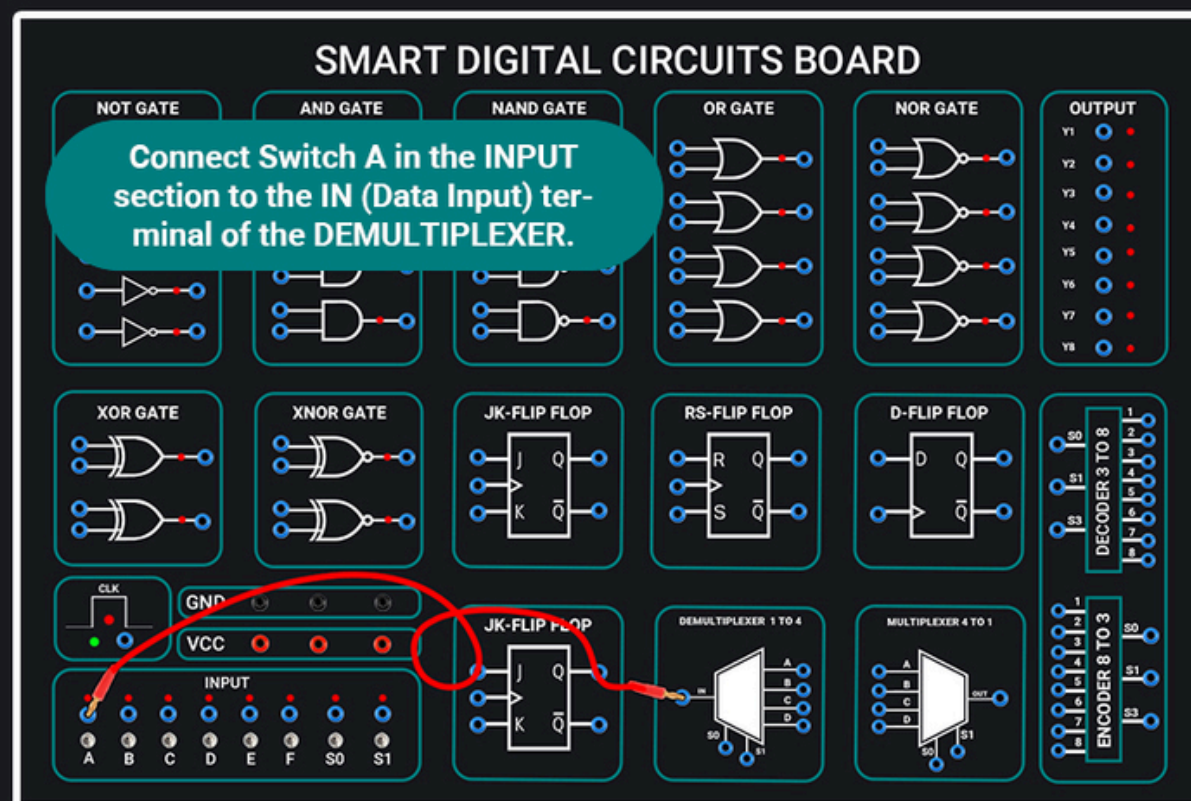


SMART DIGITAL CIRCUITS BOARD

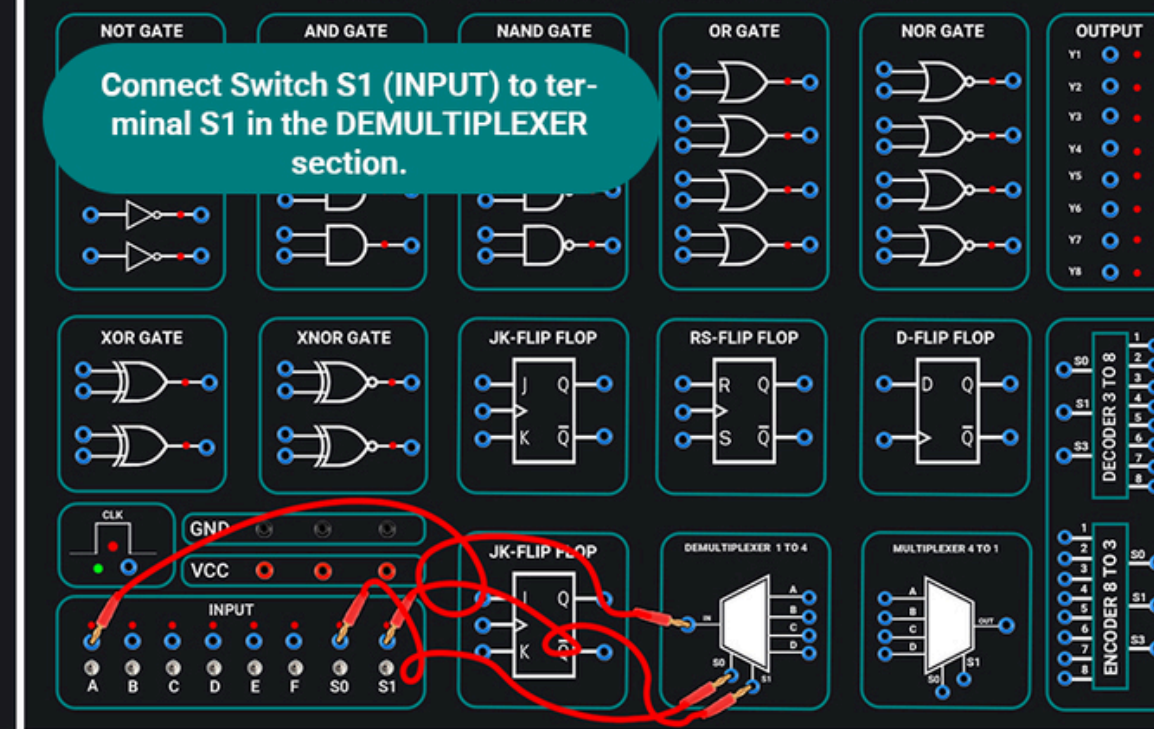Connect Switch S1 (INPUT) to terminal S1 in the DEMULTIPLEXER section.




3

2

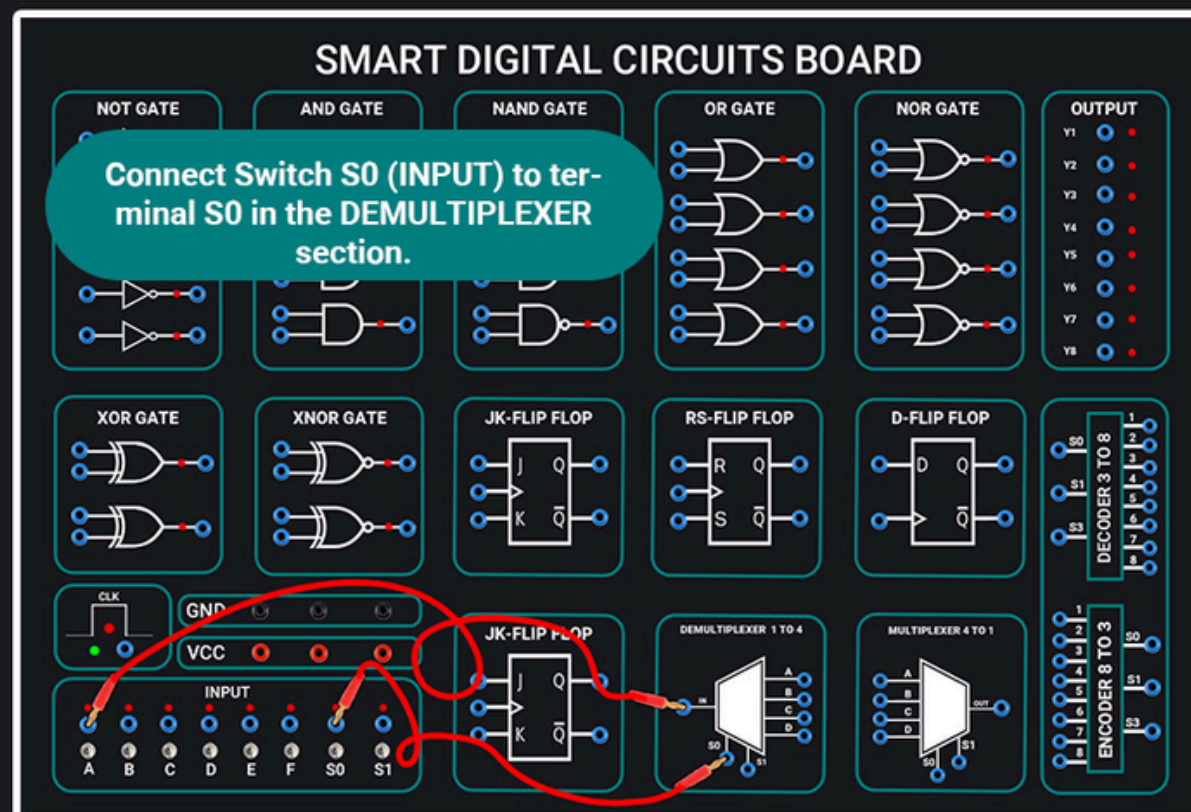

SMART DIGITAL CIRCUITS BOARD

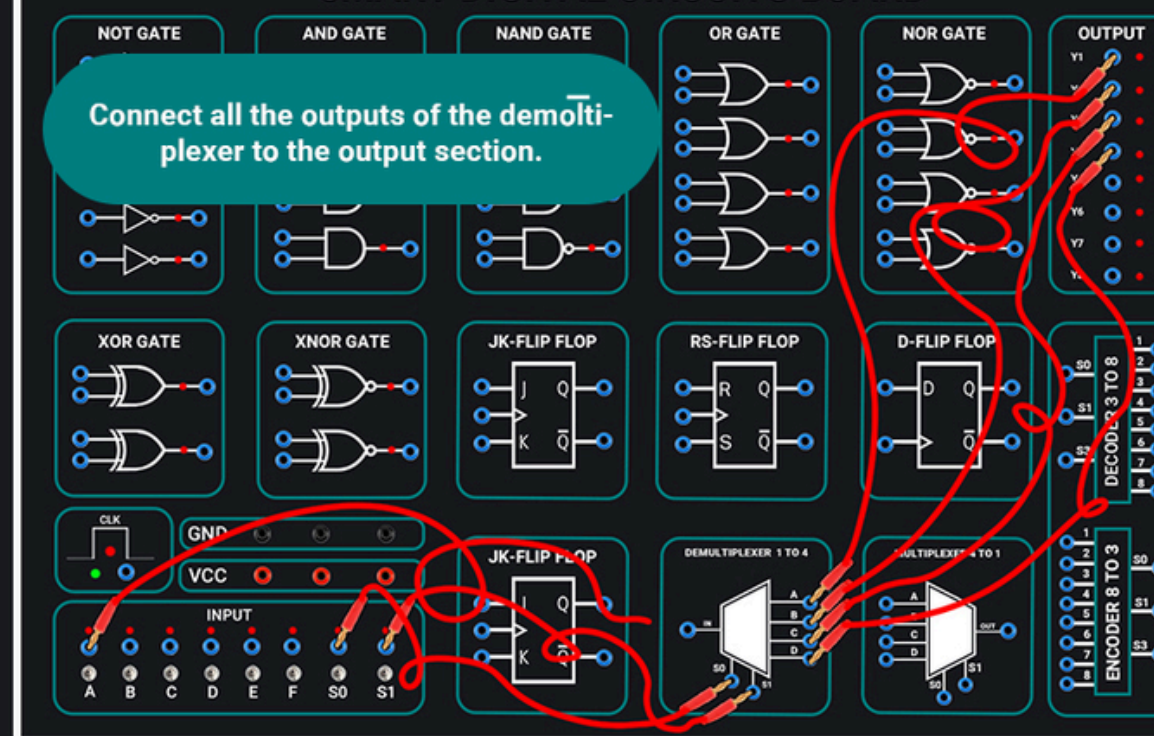Connect all the outputs of the demultiplexer to the output section.



4

SMART DIGITAL CIRCUITS BOARD

