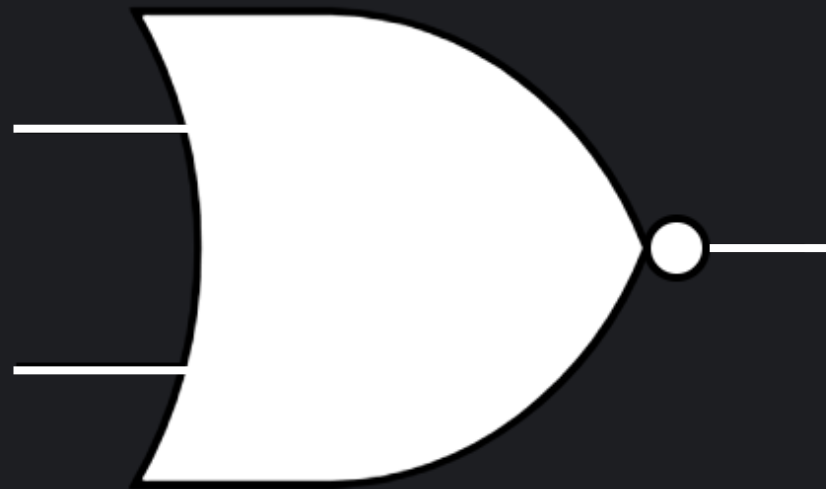



NOR GATE



What is a NOR Gate?

A NOR gate is a basic logic gate that produces a LOW (0) output when any of its inputs (or all of them) are HIGH. The output is HIGH (1) only when all inputs are LOW (0).

Truth Table

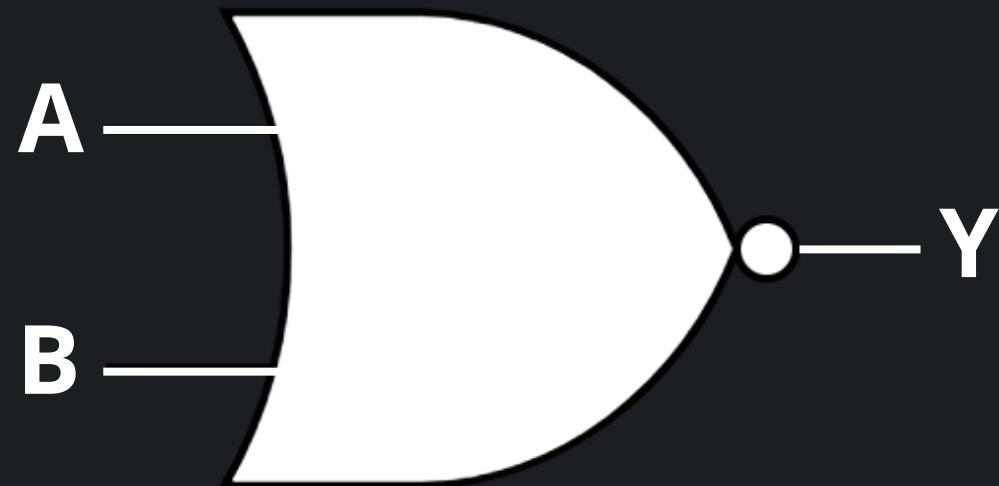


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Function of the NOR Gate

A NOR gate performs a logical NOR (Negated OR) operation on its inputs. The main function of a NOR gate is to combine two or more input signals and produce an output signal according to this rule:


Output = 0 when any input (or all inputs) = 1

Output = 1 only when all inputs = 0

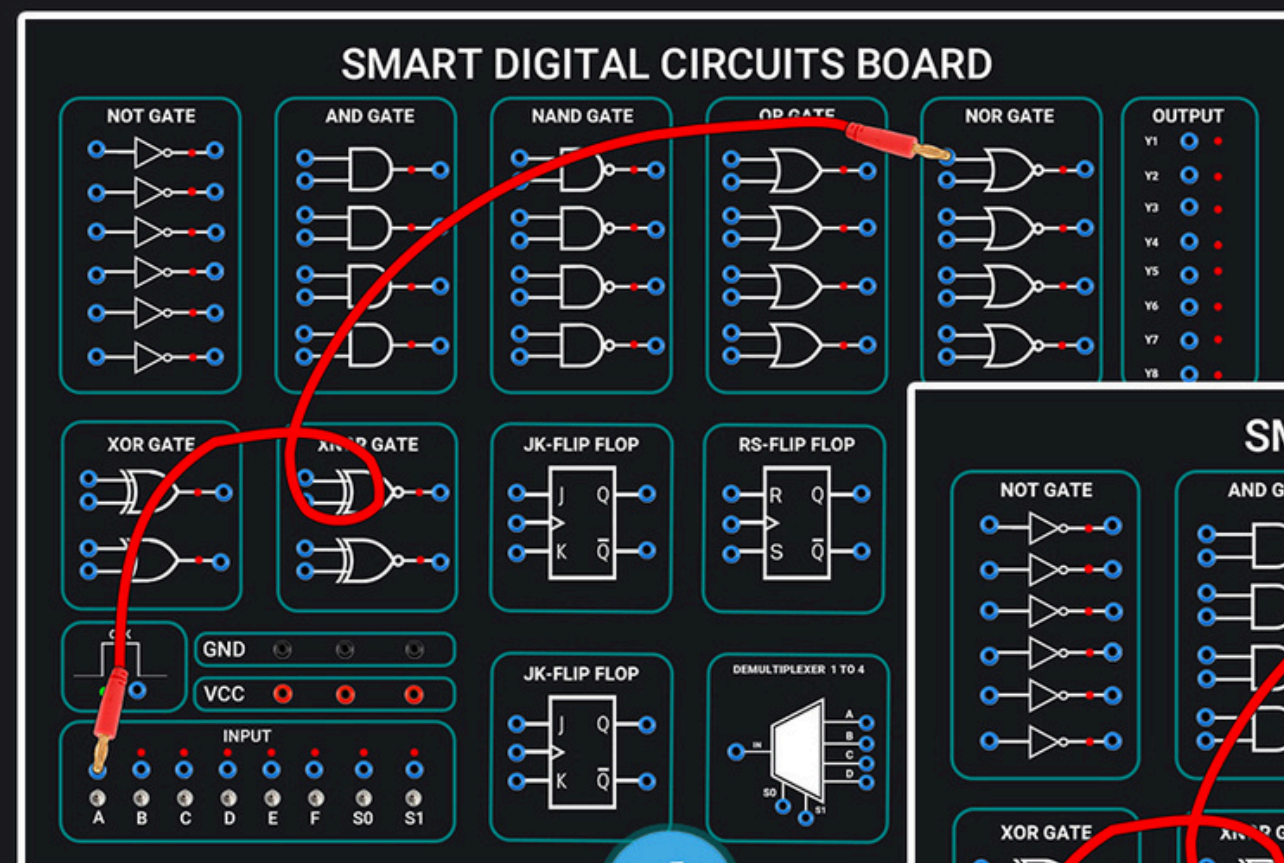

1

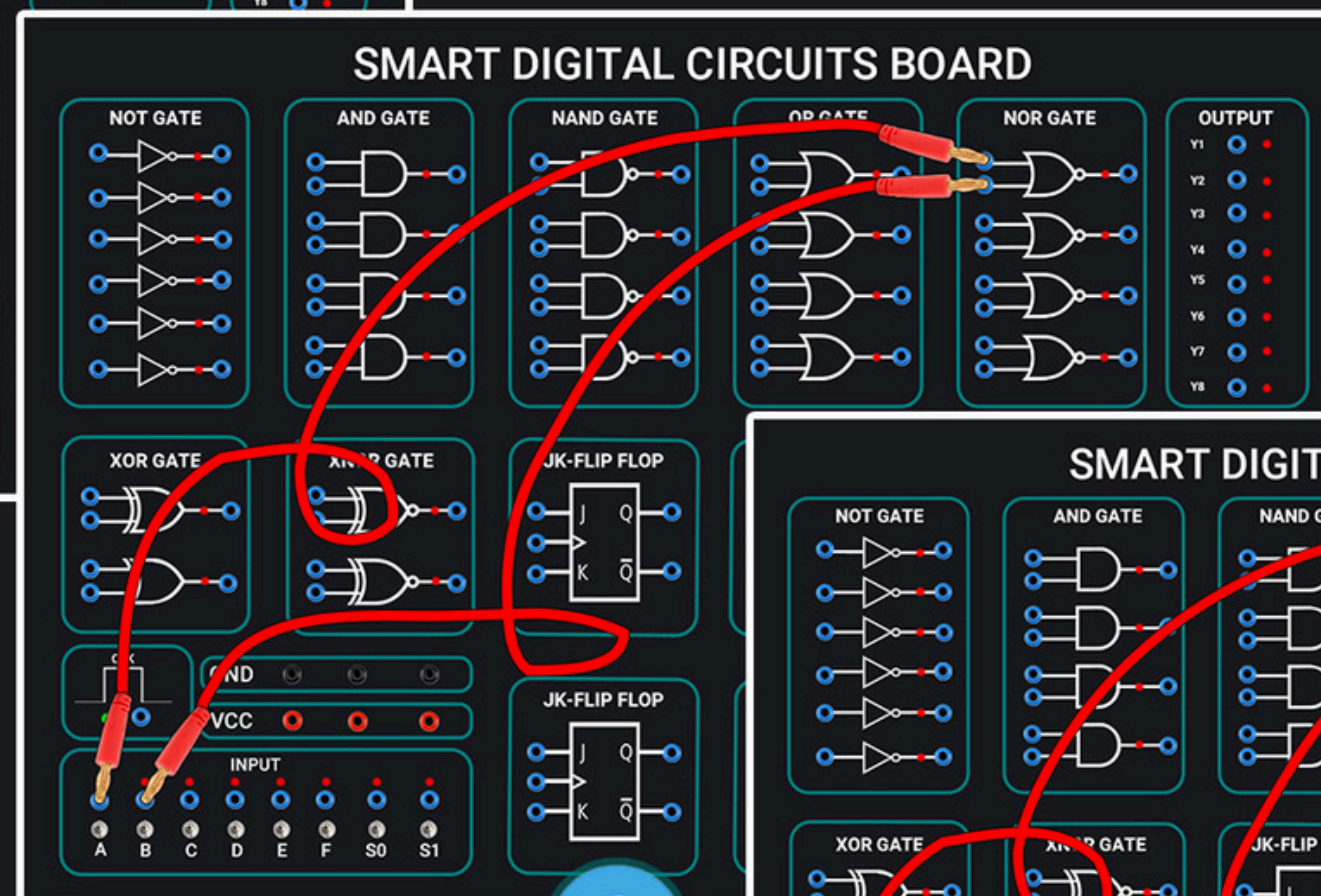Connect a wire from the first input (top blue terminal) to switch A in the INPUT section.




2

Connect a wire from the second input (bottom blue terminal) to switch B in the INPUT section

Connect the NOR Gate

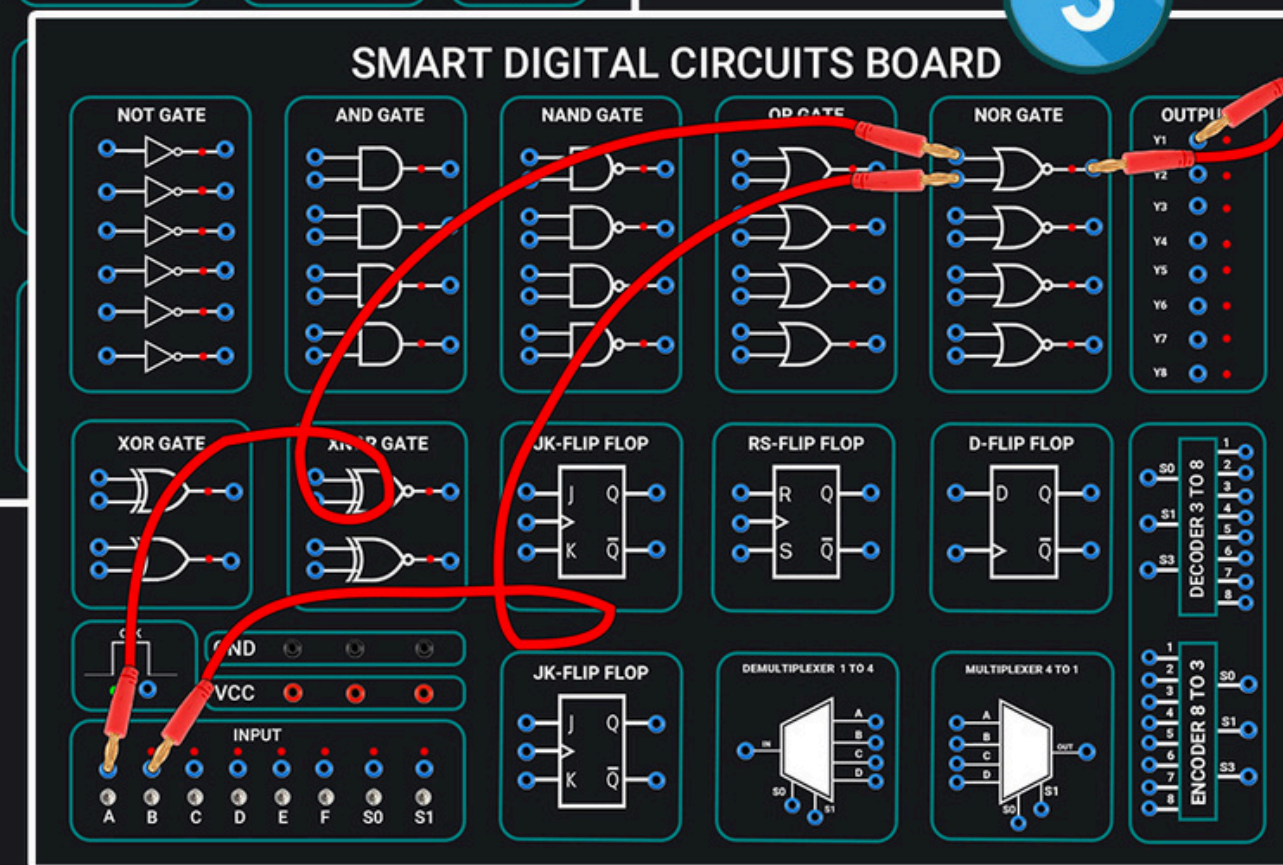Connect a wire from the gate output to terminal Y1 (or any point from Y1 to Y8) in the OUTPUT section at the top right.



SMART DIGITAL CIRCUITS BOARD

