

OR Gate



What is a NAND Gate?

An OR gate is a basic logic gate that produces a HIGH (1) output when any of its inputs (or all of them) are HIGH. The output is LOW (0) only when all inputs are LOW (0).

Truth Table



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


Function of the OR Gate

An OR gate performs a logical addition (disjunction) operation on its inputs.

The main function of an OR gate is to combine two or more input signals and produce an output signal according to this rule:


Output = 1 when any input (or all inputs) = 1

Output = 0 only when all inputs = 0

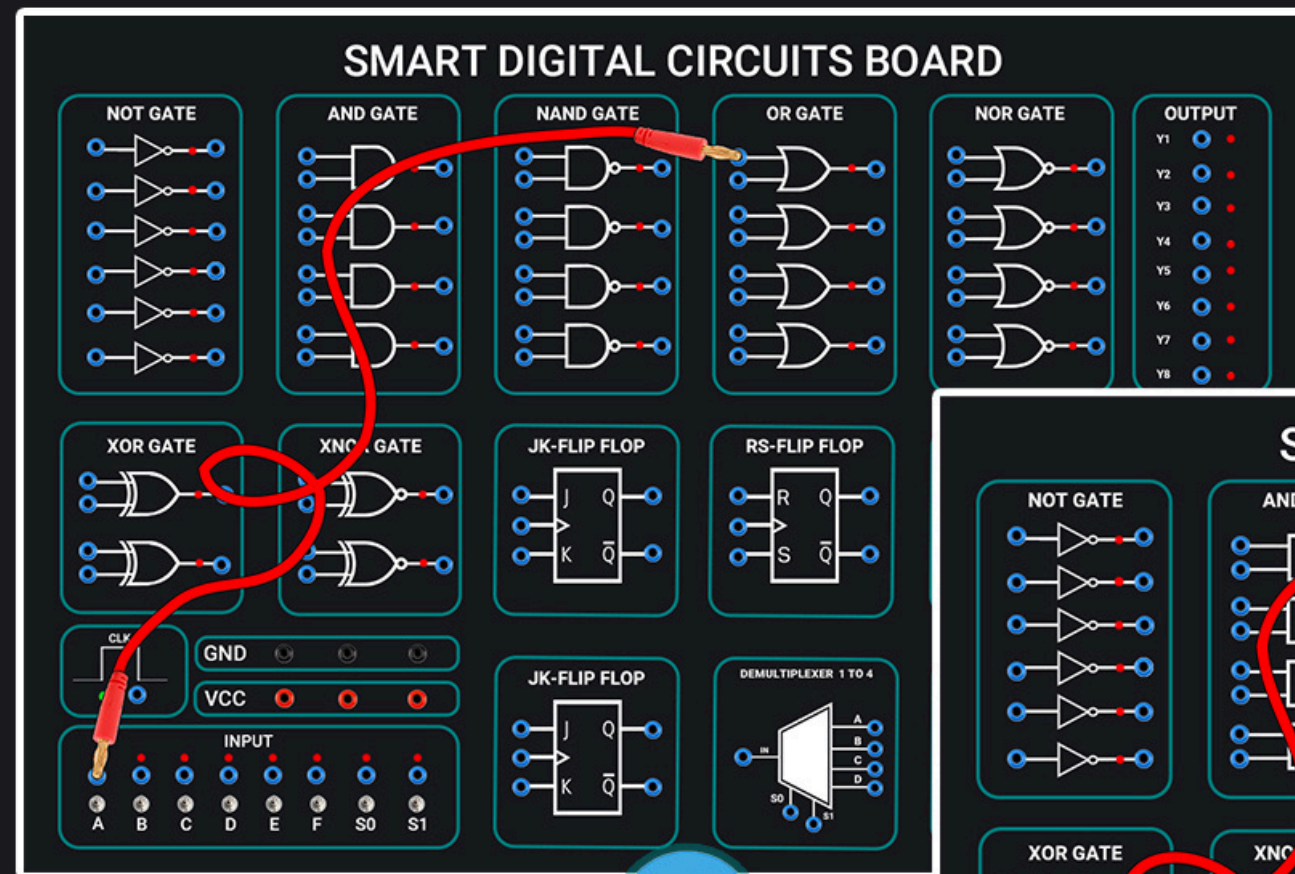

1

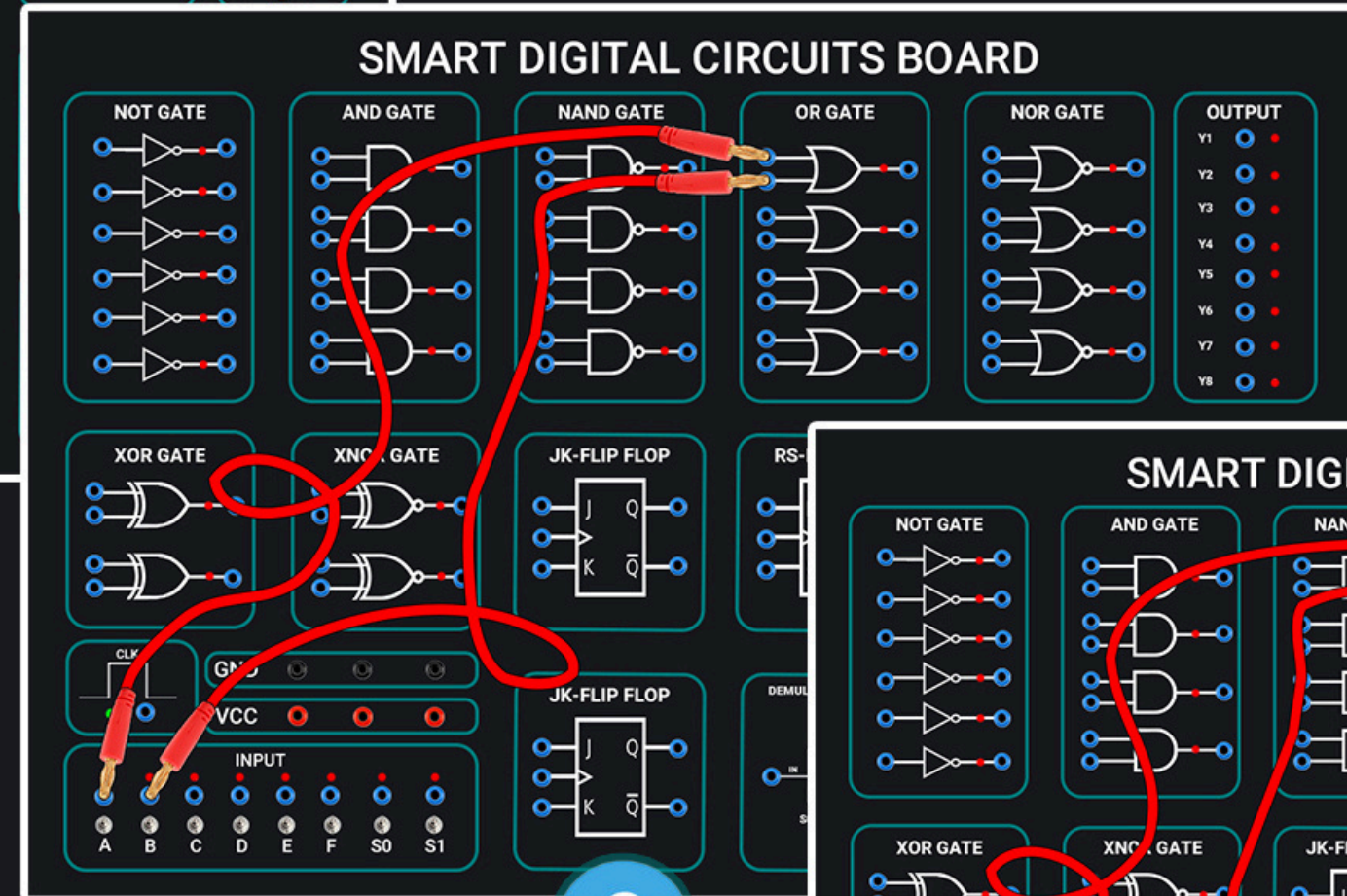Connect a wire from the first input (top blue terminal) to switch A in the INPUT section.




2

Connect a wire from the second input (bottom blue terminal) to switch B in the INPUT section

Connect the OR Gate

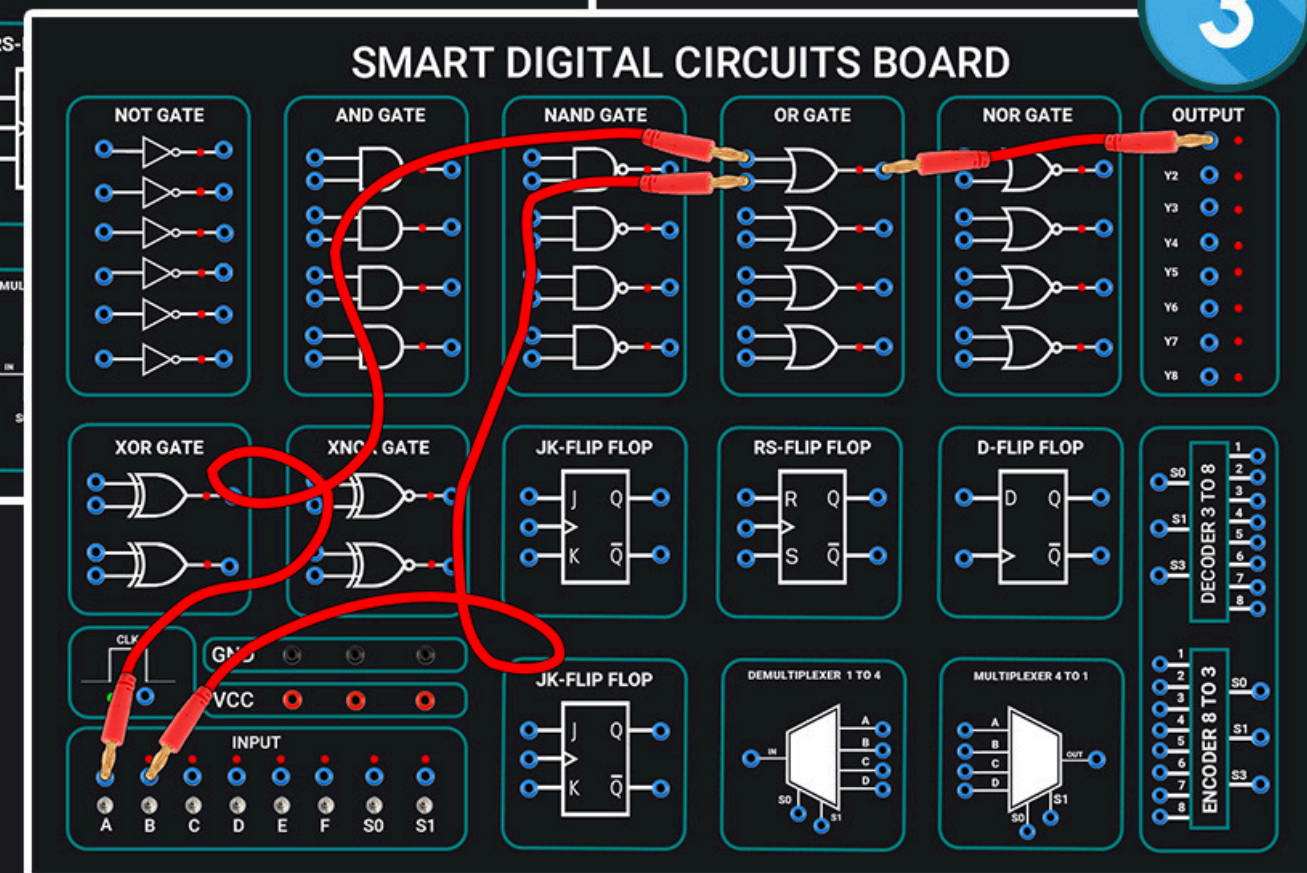Connect a wire from the gate output to terminal Y1 (or any point from Y1 to Y8) in the OUTPUT section at the top right.



3

SMART DIGITAL CIRCUITS BOARD

