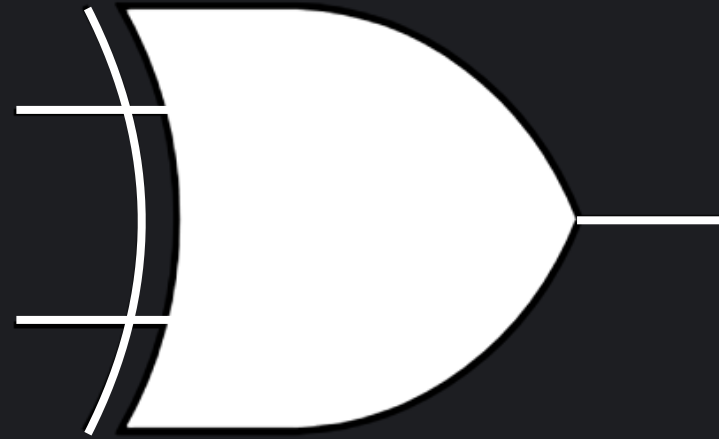



XOR GATE



What is a XOR Gate?

An XOR gate is a basic logic gate that produces a HIGH (1) output when its inputs are different. The output is LOW (0) when all inputs are the same (either all LOW or all HIGH).

Truth Table

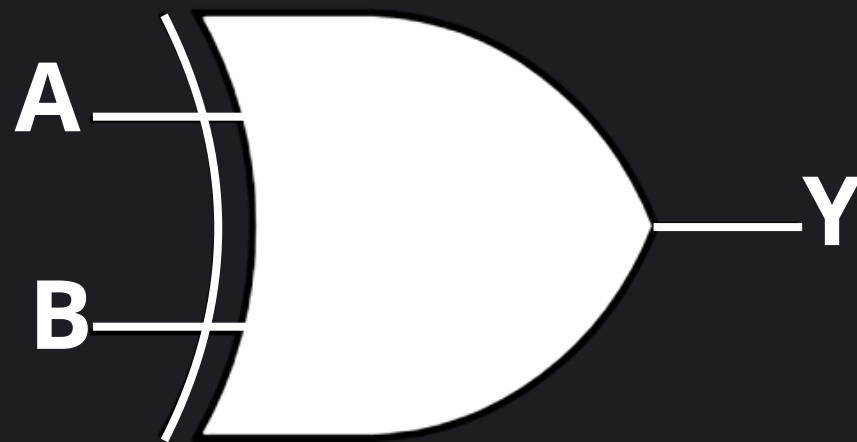

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Function of the XOR Gate

An XOR gate performs a logical Exclusive OR (XOR) operation on its inputs. The main function of an XOR gate is to combine two or more input signals and produce an output signal according to this rule:

Output = 1 when the inputs are different


Output = 0 when the inputs are the same (either all 0 or all 1)

-

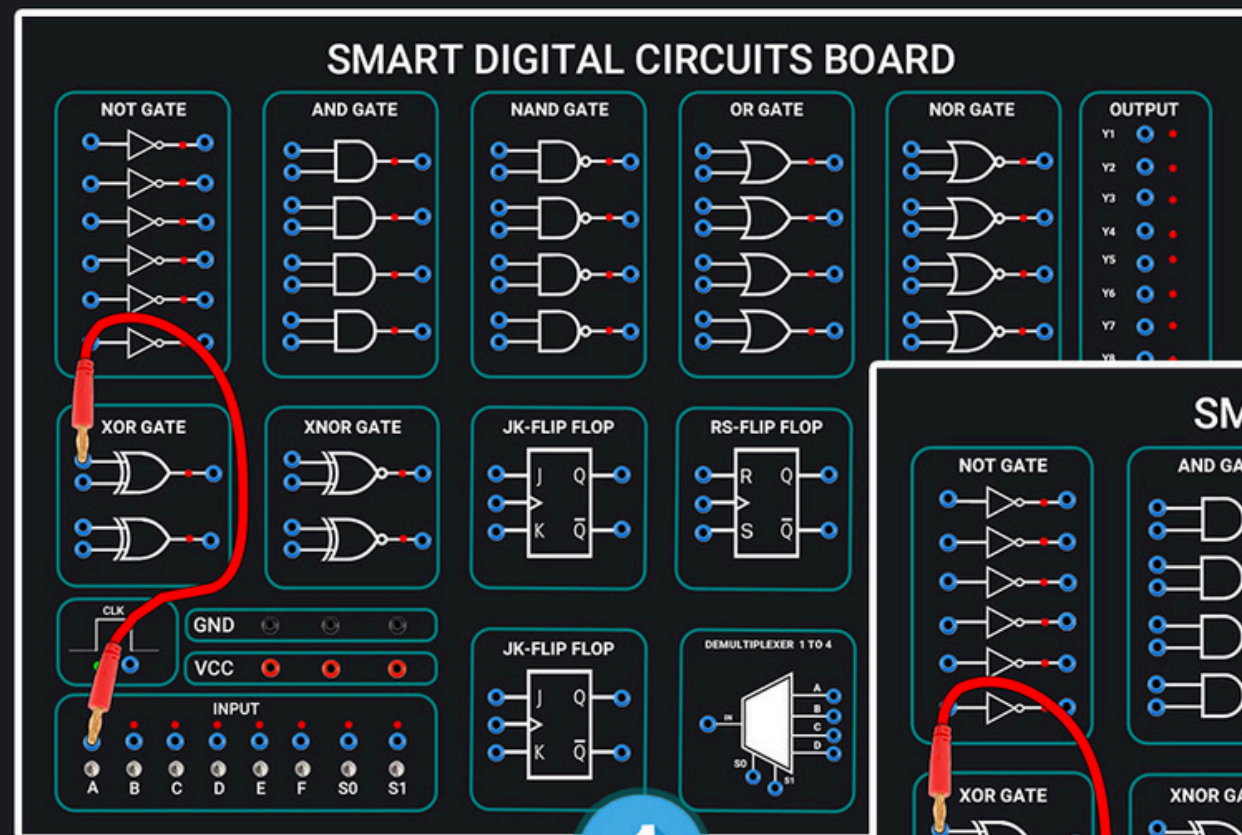

1

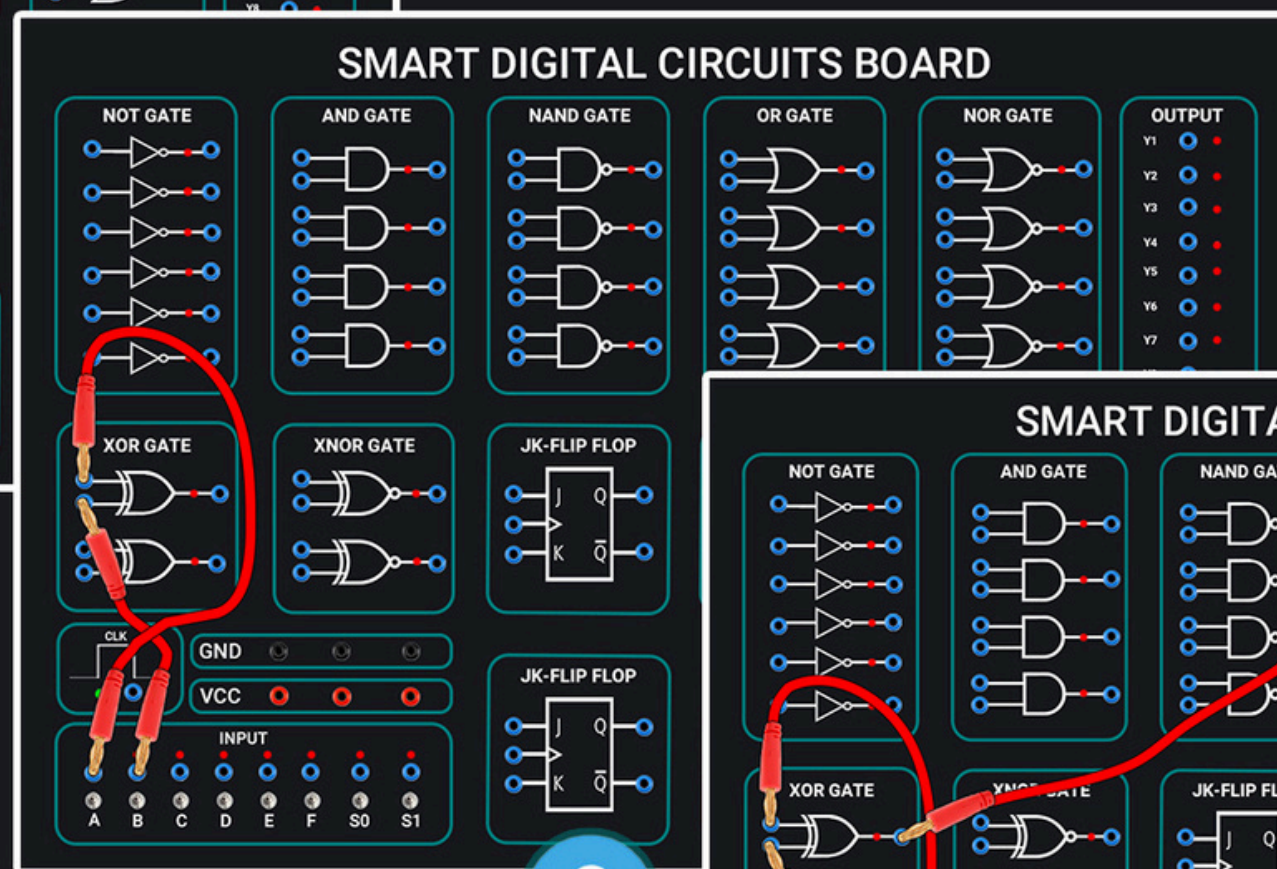Connect a wire from the first input (top blue terminal) to switch A in the INPUT section.




2

Connect a wire from the second input (bottom blue terminal) to switch B in the INPUT section

Connect the XOR Gate


3

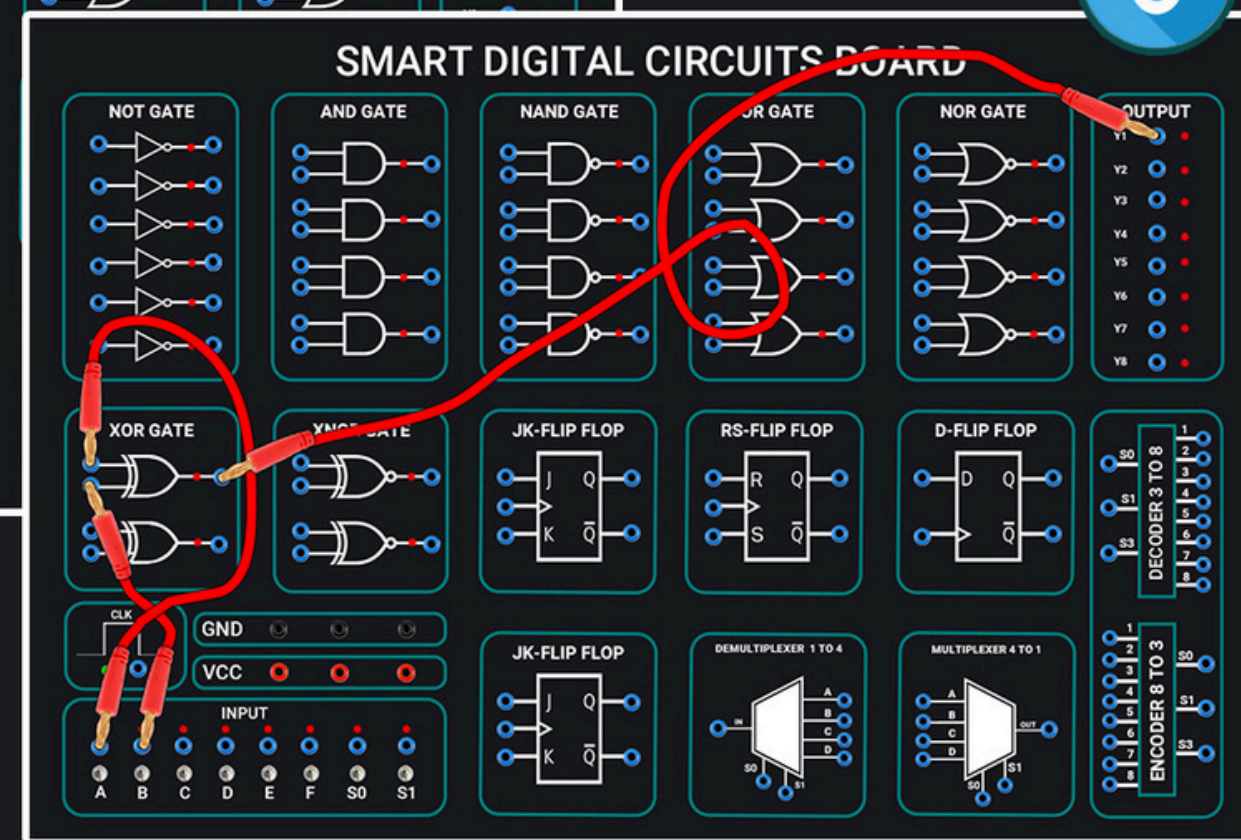Connect a wire from the gate output to terminal Y1 (or any point from Y1 to Y8) in the OUTPUT section at the top right.




SMART DIGITAL CIRCUITS BOARD


NOT GATE

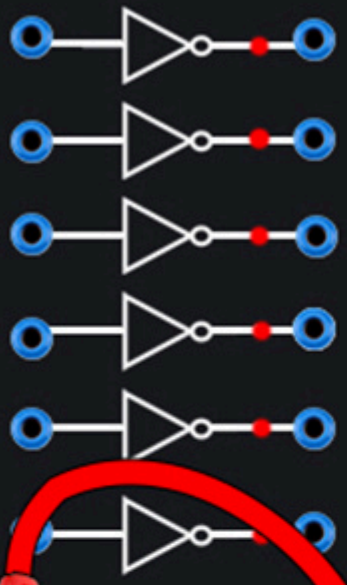


AND GATE

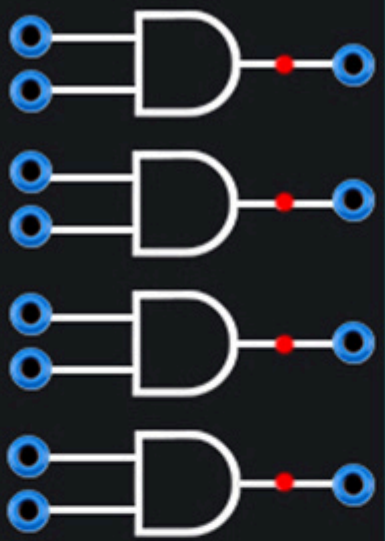


NAND GATE

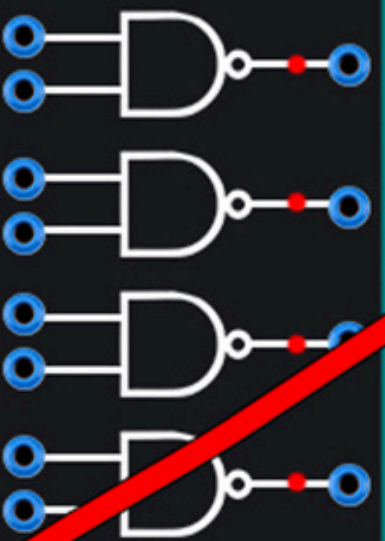

OR GATE

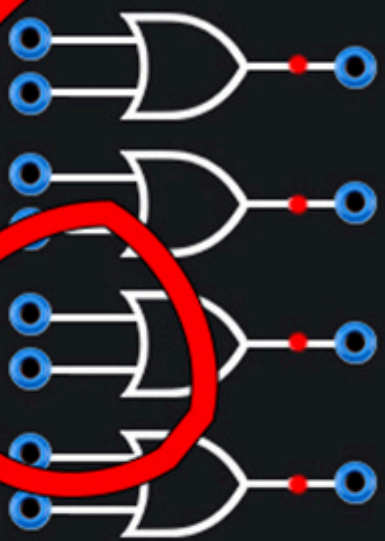


NOR GATE

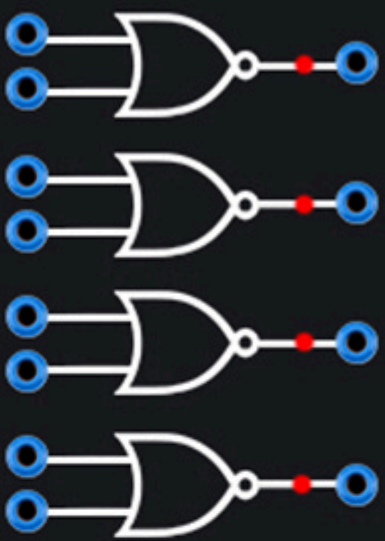


OUTPUT

Y1		
Y2		
Y3		
Y4		
Y5		
Y6		
Y7		
Y8		


XOR GATE

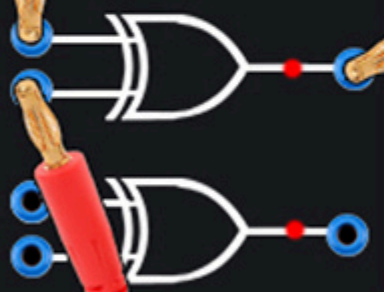


XNOR GATE

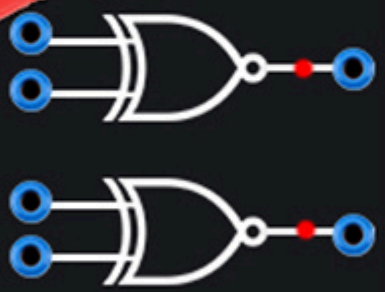


JK-FLIP FLOP

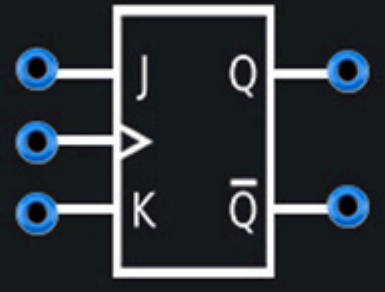

RS-FLIP FLOP

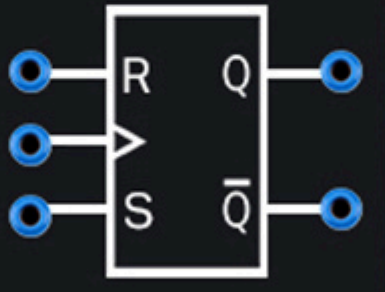

D-FLIP FLOP

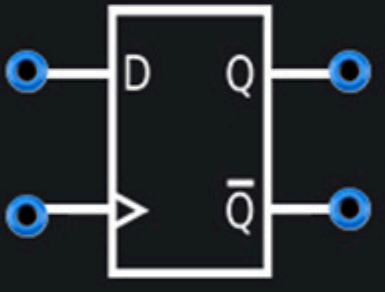

DECODE 3 TO 8

S0	1
S1	2
S2	3
S3	4
	5
	6
	7
	8

CLK



GND




VCC




INPUT

A	B	C	D	E	F	S0	S1
---	---	---	---	---	---	----	----


JK-FLIP FLOP

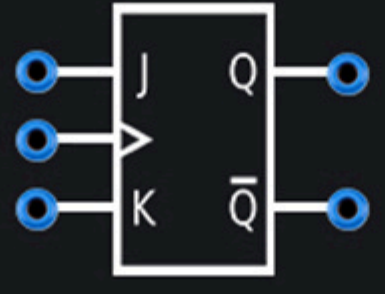

DEMULTIPLEXER 1 TO 4

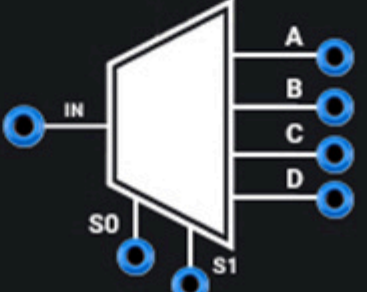

MULTIPLEXER 4 TO 1

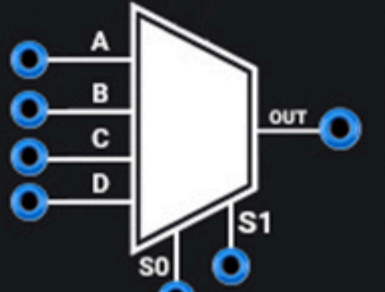

ENCODE 8 TO 3

1	S0
2	S1
3	S2
4	S3
5	
6	
7	
8	

